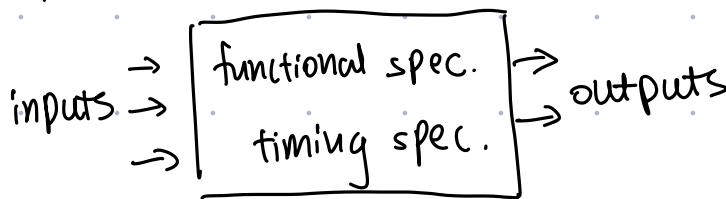


Logic Circuits


↳ Composed of



↳ high-level classification.

- **Nodes**

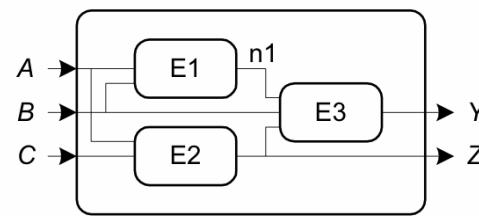- Inputs: A, B, C
- Outputs: Y, Z
- Internal: n1



- **Circuit elements**

- E1, E2, E3
- Each a circuit


↳ types of logic circuits.

↳ combinational → no memory
→ output depends on current val of inputs.

↳ sequential → memory
→ outputs dep. on current & prev inputs.

Rules of Combinational Composition

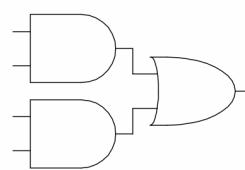- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
- Example:




Boolean Equations

this is an adder

- Functional specification of outputs in terms of inputs

- Example:** $S = F(A, B, C_{in})$
 $C_{out} = F(A, B, C_{in})$

$$0+1=1$$

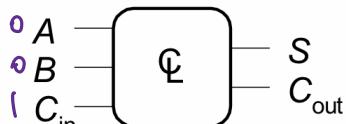

$$\begin{aligned} S &= A \oplus B \oplus C_{in} \\ C_{out} &= AB + AC_{in} + BC_{in} \end{aligned}$$

$$0+1=1 \quad \frac{01}{2^1} \frac{1}{2^0}$$

© Digital Design and Computer Architecture, 2nd Edition, 2012



Some Definitions

- Variable:** A, B, C... (without bars)
- Complement:** variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- Literal:** variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- Implicant:** product of literals
 $ABC, \bar{A}C, BC$
- Minterm:** product that includes all input variables
 $ABC, \bar{A}\bar{B}\bar{C}, \bar{A}BC$
- Maxterm:** sum that includes all input variables
 $(A+\bar{B}+C), (\bar{A}+B+\bar{C}), (\bar{A}+\bar{B}+C)$



Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)
- Form function by **ORing** minterms where **output is 1**
- Thus, a **sum** (OR) of products (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\bar{A} \bar{B}$	m_0
0	1	1	$\bar{A} B$	m_1
1	0	0	$A \bar{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \overline{AB} + AB = \Sigma(1, 3)$$



© Digital Design and Computer Architecture, 2nd Edition, 2012

AND AND
OR

Product-of-Sums (POS) Form

- we are defining a different way because we want the default outcome to give us the desired outcome.*
- All Boolean equations can be written in POS form
 - Each row has a **maxterm**
 - A maxterm is a **sum** (OR) of literals
 - Each maxterm is **FALSE** for that row (and only that row)
 - Form function by **ANDing** maxterms where **output is 0**
 - Thus, a **product** (AND) of sums (OR terms)

A=0

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \bar{B}$	M_1
1	0	0	$\bar{A} + B$	M_2
1	1	1	$\bar{A} + \bar{B}$	M_3

$$Y = F(A, B) = (A + B)(\bar{A} + \bar{B}) = \Pi(0, 2)$$



© Digital Design and Computer Architecture, 2nd Edition, 2012

The 2 forms are related $\bar{A}\bar{B} + A\bar{B} = (\bar{A} + B)(\bar{A} + \bar{B})$

An example.

SOP & POS Form

- **SOP** – sum-of-products

O	C	E	minterm
0	0	0	$\bar{O} \bar{C}$
0	1	0	$\bar{O} C$
1	0	1	$O \bar{C}$
1	1	0	$O C$

$$E = O\bar{C}$$
$$= \Sigma(2)$$

- **POS** – product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \bar{C}$
1	0	1	$\bar{O} + C$
1	1	0	$\bar{O} + \bar{C}$


$$E = (O + C)(O + \bar{C})(\bar{O} + C)$$
$$= \Pi(0, 1, 3)$$



An example of multiple-output circuit.

Priority Circuit Hardware

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

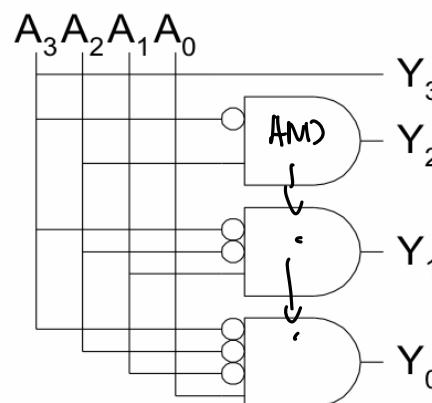

~~X~~-Notation:

Don't Cares: X

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0


A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	1	X	1
0	1	0	X	0	1	X	1
0	1	1	X	0	1	X	1
1	0	0	X	0	1	X	1
1	0	1	X	0	1	X	1
1	1	0	X	0	1	X	1
1	1	1	X	0	1	X	1

© Digital Design and Computer Architecture, 2nd Edition, 2012



Contention: X

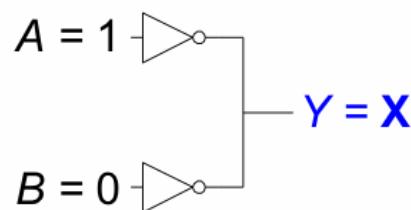- Contention: circuit tries to drive output to 1 **and** 0
 - Actual value somewhere in between
 - Could be 0, 1, or in forbidden zone
 - Might change with voltage, temperature, time, noise
 - Often causes excessive power dissipation



- Warnings:**
 - Contention usually indicates a **bug**.
 - X is used for**
 - “don’t care” in a truth table
 - and contention in logic simulation


© Digital Design and Computer Architecture, 2nd Edition, 2012



Floating - Z

Floating: Z

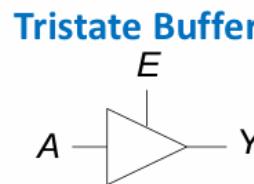- Floating, high impedance, open, high Z
- Floating output might be 0, 1, or somewhere in between
 - A voltmeter won't indicate whether a node is floating



E	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1


© Digital Design and Computer Architecture, 2nd Edition, 2012



Tristate Busses

- Floating nodes are used in tristate busses
 - Many different drivers
 - Exactly one is active at once

*Z's value is
set by the bus's
state.*

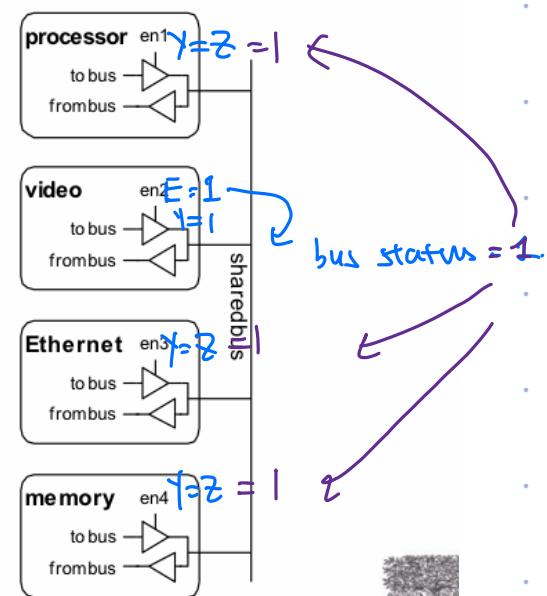

© Digital Design and Computer Architecture, 2nd Edition, 2012



Boolean Algebra

Boolean Axioms

Boolean Axioms

Number	Axiom	Dual	Name
A1	$B = 0 \text{ if } B \neq 1$	$B = 1 \text{ if } B \neq 0$	Binary Field
A2	$0 = \bar{1}$	$1 = \bar{0}$	NOT
A3	$0 \bullet 0 = 0$	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	$1 + 0 = 0 + 1 = 1$	AND/OR

Dual: Replace: • with +
0 with 1

© Digital Design and Computer Architecture, 2nd Edition, 2012.



Boolean Theorems of One Variable

Number	Theorem	Name
T1	$B \bullet 1 = B$	Identity
T2	$B \bullet 0 = 0$	Null Element
T3	$B \bullet B = B$	Idempotency
T4	$\bar{\bar{B}} = B$	Involution
T5	$B \bullet \bar{B} = 0$	Complements

© Digital Design and Computer Architecture, 2nd Edition, 2012.



Boolean Theorems of One Variable

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4		$\bar{\bar{B}} = B$	Involution
T5	$B \bullet \bar{B} = 0$	$B + \bar{B} = 1$	Complements

Dual: Replace: • with +
0 with 1

T1: Identity Theorem

$$B \cdot 1 = B, \quad B + 0 = B$$

T2: Null Element Theorem

$$B \cdot 0 = 0, \quad B + 1 = 1$$

T3: Idempotency Theorem

$$B \cdot B = B, \quad B + B = B$$

T4: Identity Theorem

$$\bar{\bar{B}} = B, \quad B \cdot 0 \cdot \bar{D} = B$$

T5: Complement Theorem

$$\bar{B} \cdot \bar{B} = 0$$

$$\frac{B}{B} = 1$$