

 
 
 


logic gates.

 


XOR

 


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

NAND

 


NOR

 

XNOR


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

NOR3

 


A	B	C	Y
0	0	0	1
...	0
...	0

AND3

 



XOR3

 

(Outputs 1 when an odd # of inputs is 1.)

Noise

- Anything that degrades the signal.

  


$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{OL} - V_{IL}$$


DC Transfer Characteristics

Ideal Buffer:

 

$$NM_H = NM_L = V_{DD}/2$$

Real Buffer:

 


$$NM_H, NM_L < V_{DD}/2$$



Transistors

 - ↳ building blocks for logic gates.
- ↳ 3 ported voltage-controlled switch.




↳ 2 types of transistors: nmos & pmos.

	$V=0$	$V=1$
nmos	0	1
pmos	1	0


pass good 0's: connect source to GND
pass good 1's: connect source to VDD

Using Transistors to build gates

① NOT Gate:

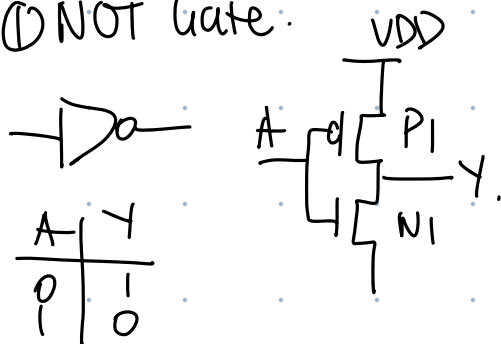


② NAND GATE

 


③ AND2 GATE

$= D$


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

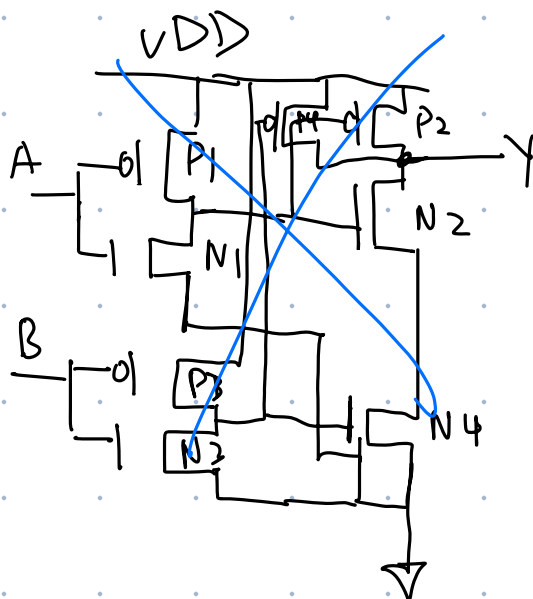

should be
NAND+NOT,
not NOT+NAND

 


④ NOR3 Gate

 

★ It is easier to
build inversion gates
with CMOS transistors.

Transmission Gate

 

controlled by complementary signals.

ensures that the nMOS & pMOS are on & off together.