

ECE 2011

Introduction to Computer Engineering
Spring 2026

Lecture 17

03-31-2026

Linghao Song


Yale ECE

Assignment 4

- Sign up
- https://docs.google.com/spreadsheets/d/1ezydqTY5wrlBKDSLpwee_e9xpLkA4WnUzkj0U1XD2fU/edit?gid=0#gid=0

Assignment 4 Sign-Up Sheet: Paper Presentation Groups.						
Topic	Paper	Member 1	Member 2	Member 3	Member 4	Member 5 (use c
Topic 1: Evolution of Google TPU Architectures	TPU (ISCA 2017)					
Topic 1: Evolution of Google TPU Architectures	TPU v4 (ISCA 2023)					
Topic 2: Efficient LLM Inference on Specialized Hardware	Splitwise (ISCA 2024)					
Topic 2: Efficient LLM Inference on Specialized Hardware	FlightLLM (FPGA 2024)					
Topic 3: Vision Transformer Acceleration	HeatViT (HPCA 2023)					
Topic 3: Vision Transformer Acceleration	ViTCoD (HPCA 2023)					
Topic 4: FPGA CAD and Compilation	AutoBridge (FPGA 2021)					
Topic 4: FPGA CAD and Compilation	ARIES (FPGA 2025)					
Topic 5: FPGA Architectures for Scientific Compute	Callipepla (FPGA 2023)					
Topic 5: FPGA Architectures for Scientific Compute	Du et al (FPGA 2022)					
Short name	Full title	Conference	Year	DOI / URL		
TPU (ISCA 2017)	In-Datacenter Performance Analysis of a Tensor Processing Unit	ISCA	2017	https://arxiv.org/abs/1704.04760		
TPU v4 (ISCA 2023)	TPU v4: An Optically Reconfigurable Supercomputer for Machine Learning with Hardware Support for Embedding	ISCA	2023	https://arxiv.org/abs/2304.01433		
Splitwise (ISCA 2024)	Splitwise: Efficient Generative LLM Inference Using Phase Splitting	ISCA	2024	https://doi.org/10.1109/ISCA59077.2024.00019		
FlightLLM (FPGA 2024)	FlightLLM: Efficient Large Language Model Inference with a Complete Mapping Flow on FPGAs	FPGA	2024	https://arxiv.org/abs/2401.03868		
HeatViT (HPCA 2023)	HeatViT: Hardware-Efficient Adaptive Token Pruning for Vision Transformers	HPCA	2023	https://doi.org/10.1109/HPCA56546.2023.10071047		
ViTCoD (HPCA 2023)	ViTCoD: Vision Transformer Acceleration via Dedicated Algorithm and Accelerator Co-Design	HPCA	2023	https://doi.org/10.1109/HPCA56546.2023.10071027		
AutoBridge (FPGA 2021)	AutoBridge: Coupling Coarse-Grained Floorplanning and Pipelining for High-Frequency HLS Design on Multi-Die	FPGA	2021	https://doi.org/10.1145/3431920.3439289		
ARIES (FPGA 2025)	ARIES: An Agile MLIR-Based Compilation Flow for Reconfigurable Devices with AI Engines	FPGA	2025	https://doi.org/10.1145/3706628.3708870		
Callipepla (FPGA 2023)	Callipepla: Stream Centric Instruction Set and Mixed Precision for Accelerating Conjugate Gradient Solver	FPGA	2023	https://doi.org/10.1145/3543622.3573182		
Du et al (FPGA 2022)	High-Performance Sparse Linear Algebra on HBM-Equipped FPGAs Using HLS: A Case Study on SpMV	FPGA	2022	https://doi.org/10.1145/3490422.3502368		


Single-Cycle Processor

 

R-Type

- *Register-type*
- 3 register operands:
 - rs, rt: source registers
 - rd: destination register
- Other fields:
 - op: the *operation code* or *opcode* (0 for R-type instructions)
 - funct: the *function*
with opcode, tells computer what operation to perform
 - shamt: the *shift amount* for shift instructions, otherwise it's 0


R-Type

 

I-Type

- *Immediate-type*
- 3 operands:
 - `rs, rt`: register operands
 - `imm`: 16-bit two's complement immediate
- Other fields:
 - `op`: the opcode
 - Simplicity favors regularity: all instructions have opcode
 - Operation is completely determined by opcode


I-Type

 

Machine Language: J-Type

- *Jump-type*
- 26-bit address operand (`addr`)
- Used for jump instructions (`j`)

J-Type

 

Review: Instruction Formats

R-Type

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits


J-Type

op	addr
6 bits	26 bits

Architectural State

- Determines everything about a processor:
 - PC
 - 32 registers
 - Memory

MIPS State Elements

 


Single-Cycle MIPS Processor

- Datapath
- Control


Single-Cycle Datapath: 1w fetch

STEP 1: Fetch instruction

 

Single-Cycle Datapath: lw Register Read

STEP 2: Read source operands from RF

 


$lw \$s0, 20(\$s1)$

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits


Single-Cycle Datapath: l_w Immediate

STEP 3: Sign-extend the immediate

 


Single-Cycle Datapath: 1w address

STEP 4: Compute the memory address

 

Single-Cycle Datapath: lw Memory Read

 - **STEP 5:** Read data from memory and write it back to register file




`lw $s0, 20($s1)`

I-Type




Single-Cycle Datapath: 1_W PC Increment

 STEP 6: Determine address of next instruction



Single-Cycle Datapath: sw

Write data in rt to memory

 


`sw $s0, 4($s1)`

I-Type



Single-Cycle Datapath: R-Type

 - Read from `rs` and `rt`
- Write *ALUResult* to register file
- Write to `rd` (instead of `rt`)



`add $s2, $s1, $s0`


\$s2 val = \$s1 val + \$s0 val. **R-Type**

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-Cycle Datapath: beq

- Determine whether values in `rs` and `rt` are equal
- Calculate branch target address:
 
$$\text{BTA} = (\text{sign-extended immediate} \ll 2) + (\text{PC} + 4)$$




beq \$s0, \$s1, target


I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits


Single-Cycle Processor

 


Review: ALU

 

$F_{2:0}$	Function
000	$A \& B$
001	$A \mid B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \mid \sim B$
110	$A - B$
111	SLT

 

Control Unit & ALU Decoder

 


ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)

R-Type


- *Register-type*
- 3 register operands:
 - rs, rt: source registers
 - rd: destination register
- Other fields:
 - op: the *operation code* or *opcode* (0 for R-type instructions)
 - funct: the *function*
with opcode, tells computer what operation to perform
 - shamt: the *shift amount* for shift instructions, otherwise it's 0

R-Type

 

Control Unit Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000							
lw	100011							
sw	101011							
beq	000100							

 

ALUOp_{1:0}

10




Control Unit Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00 ← add \$s0 & \$s1
sw	101011							
beq	000100							

lw \$s0, 20(\$s1)

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

 


Control Unit Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011							
beq	000100							

lw \$s0, 20(\$s1)

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

 


Control Unit Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0 1	00
sw	101011	0	X	1	0	1	X	00
beq	000100							

sw \$s0, 4(\$s1)

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

 


Control Unit Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0	00
sw	101011	0	X	1	0	1	X	00
beq	000100							

sw \$s0, 4(\$s1)

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits

 

Control Unit Main Decoder


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0 1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	X	X	01

beq \$s0, \$s1, target

I-Type

op	rs	rt	imm
6 bits	5 bits	5 bits	16 bits


address

 

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	0 1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01

Single-Cycle Datapath: or

 


or \$t0, \$t1, \$t2

R-Type

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Extended Functionality: addi

 

No change to datapath

Control Unit: addi


Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000							

Control Unit: addi

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}
R-type	000000	1	1	0	0	0	0	10
lw	100011	1	0	1	0	0	1	00
sw	101011	0	X	1	0	1	X	00
beq	000100	0	X	0	1	0	X	01
addi	001000	1	0	1	0	0	0	00

addi, \$rt, \$rs, im
add val of \$rs and im.
store value in \$rt.

Extended Functionality: j

 

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000010								

Control Unit: Main Decoder

Instruction	Op _{5:0}	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	ALUOp _{1:0}	Jump
R-type	000000	1	1	0	0	0	0	10	0
lw	100011	1	0	1	0	0	1	00	0
sw	101011	0	X	1	0	1	X	00	0
beq	000100	0	X	0	1	0	X	01	0
j	000010	0	X	X	X	0	X	XX	1

data safety